 


D Flip-flop

The D flip-flop takes one data input and updates its state Q , on a clock tick, according to the table:

D	Q	$\sim Q$
0	0	1
1	1	1




In the following Logisim diagrams, the D flip-flops update state on the falling edge (when the clock goes from high to low).

JK Flip-flop

The JK flip-flop takes two data inputs and updates its state Q , on a clock tick, according to the table:

J	K	Q	$\sim Q$

0	0	no change	
0	1	0	1
1	0	1	0
1	1	opposite	

 

In the following Logisim diagrams, the JK flip-flops update state on the falling edge (when the clock goes from high to low).

A *recognizer* accepts a binary input (typically a sequence of bits) and outputs a 1 if and only if the binary input matches a specific pattern.


You might think of a recognizer as being similar to a combination lock.

The output signal can be used to control the activation of another circuit.

We need to recognize a sequence of 4 bits, which suggests the following logical states:

- A** initial state/have not yet seen a 1
- B** last bit seen was 1, previous bit was not a 1
- C** last two bits seen were 1's
- D** last bit seen was 0; previous two bits were 1's

 
We recognize the pattern **1101** when we make a transition from state **D** back to state **B**.



Design: mapping states to labels


We need to represent each state by a binary string; a trivial mapping will do:

- A 00
- B 01
- C 10
- D 11

 

Design: state transition table

Curr State	Input	Next State	Output
0 0	0	0 0	0
0 0	1	0 1	0
0 1	0	0 0	0
0 1	1	1 0	0
1 0	0	1 1	0
1 0	1	1 0	0
1 1	0	0 0	0
1 1	1	0 1	1

 

Design: choose a flip-flop

We will choose D flip-flops, since that simplifies the derivation of the next-state equations.

It is an interesting exercise to design an alternate implementation using JK flip-flops.

Design: next-state equations

C1	C0	I	N1	N0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

$$N0 = \overline{C0} \cdot \overline{C1} \cdot I + \overline{C0} \cdot C1 \cdot \overline{I} + \overline{C0} \cdot C1 \cdot I$$

$$N1 = C0 \cdot \overline{C1} \cdot I + \overline{C0} \cdot C1 \cdot \overline{I} + \overline{C0} \cdot C1 \cdot I = C0 \cdot \overline{C1} \cdot I + \overline{C0} \cdot C1$$

Design: output equation

Curr State		Input	Output

0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$Output = C0 \cdot C1 \cdot I$$

$$N0 = \overline{C0} \cdot \overline{C1} \cdot I + \overline{C0} \cdot C1 \cdot \overline{I} + \overline{C0} \cdot C1 \cdot I$$

$$N1 = C0 \cdot \overline{C1} \cdot I + \overline{C0} \cdot C1$$

