 


We will examine a simplified MIPS implementation first, and then produce a more realistic pipelined version.


A simple, representative subset of machine instructions, shows most aspects:

- Memory reference: lw, sw
- Arithmetic/logical: add, sub, and, or, slt
- Transfer of control: beq, j



- I PC $\rightarrow$ instruction memory, fetch instruction
- II Register numbers $\rightarrow$ register file, read registers to get operand(s)
- III Depending on instruction class
 - May use ALU to calculate needed value
 - R-type: need result of specified operation
 - Load/store: need memory address to be read from/written to
 - Branch: need to compare registers AND need the branch target address
 - May access data memory
 - Load/store: access data memory to read/write value
 - Set address for next instruction fetch: PC $\leftarrow$ branch target OR PC + 4 OR jump target

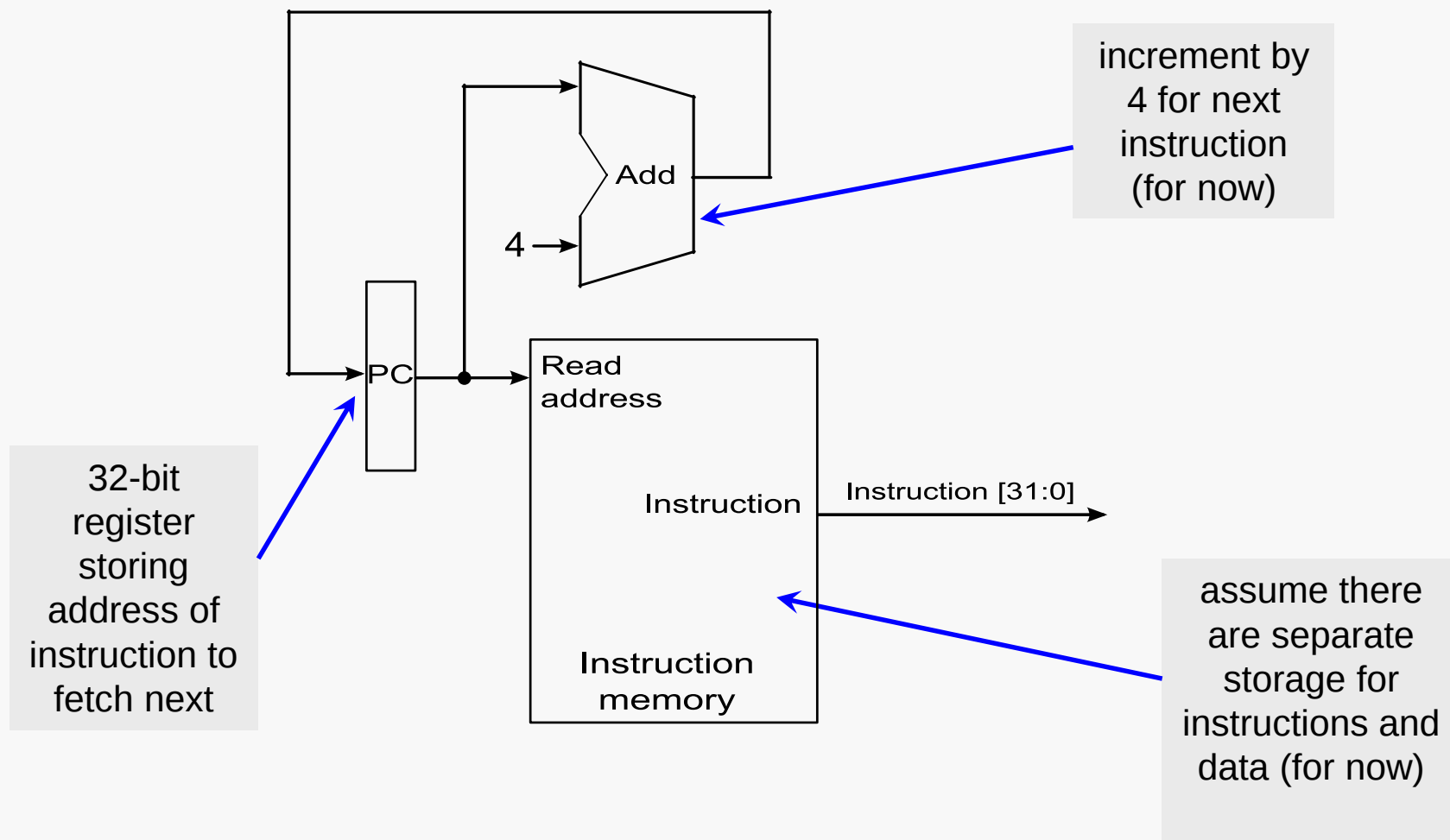Here's what we need for sequential fetches (no `beq` or `j`):




Read two operands from register file


$GPR[rd] = GPR[rs] \text{ funct } GPR[rt]$

Use ALU to perform the arithmetic/logical operation

Write the result to a register

 

 $GPR[rd] = GPR[rs] \text{ funct } GPR[rt]$




Control tells ALU Control to use the funct bits... and sets RegWrite to 1

rs and rt specify where operands are

rd specifies where result goes

add, sub, and, or, slt

 

ALU result goes to register file

ALU applies specified operation to operands


ALU Control sets ALU to correct operation

Read register operand

$$GPR[rt] = Mem[GPR[rs] + imm]$$



Calculate the address to be read using register operand and 16-bit offset from instruction

- Use ALU, but sign-extend offset

 


$$\text{GPR}[rt] = \text{Mem}[\text{GPR}[rs] + \text{imm}]$$

...
Read memory and update register

  

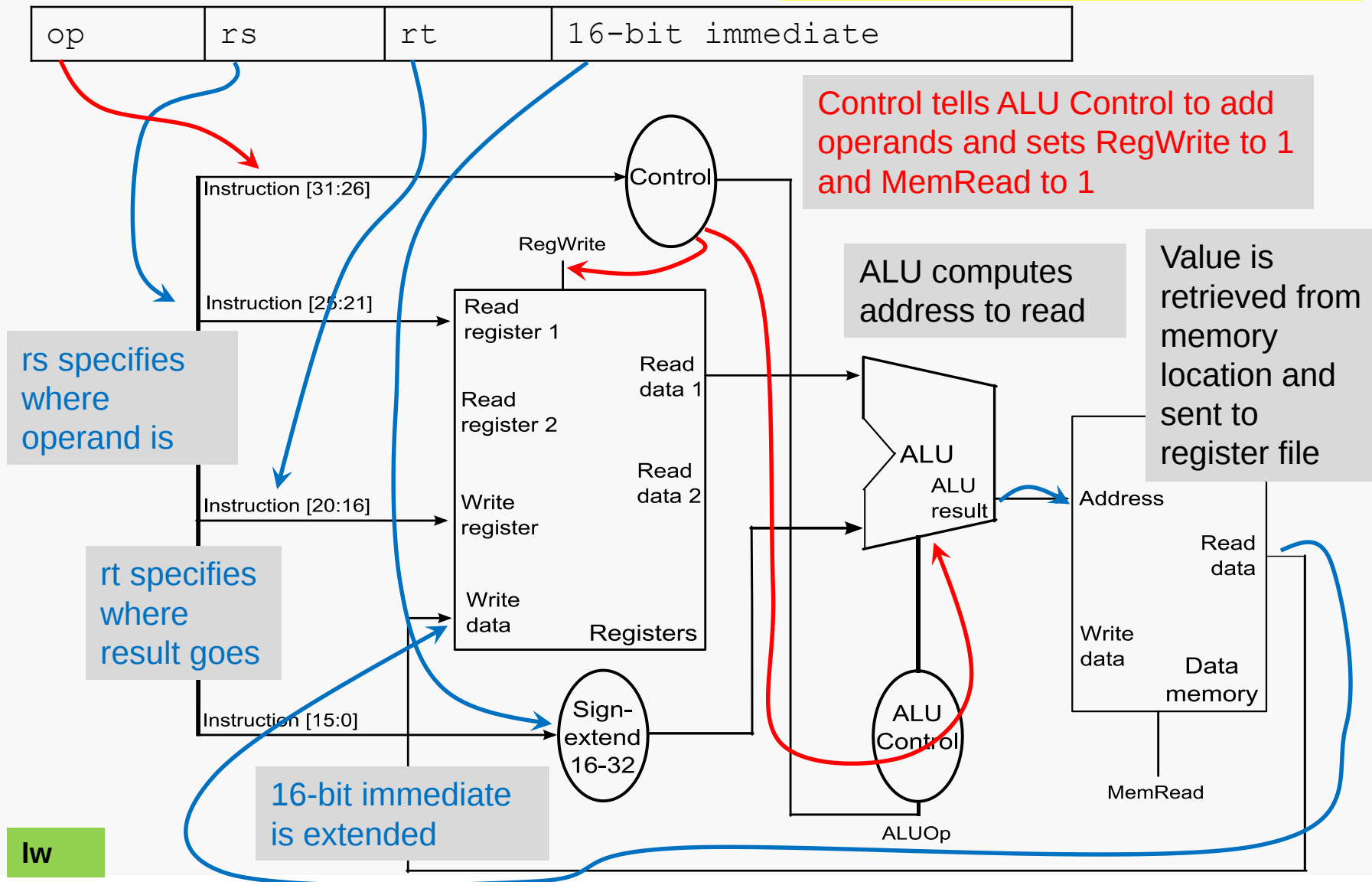
$$\text{GPR}[rt] = \text{Mem}[\text{GPR}[rs] + \text{imm}]$$



lw
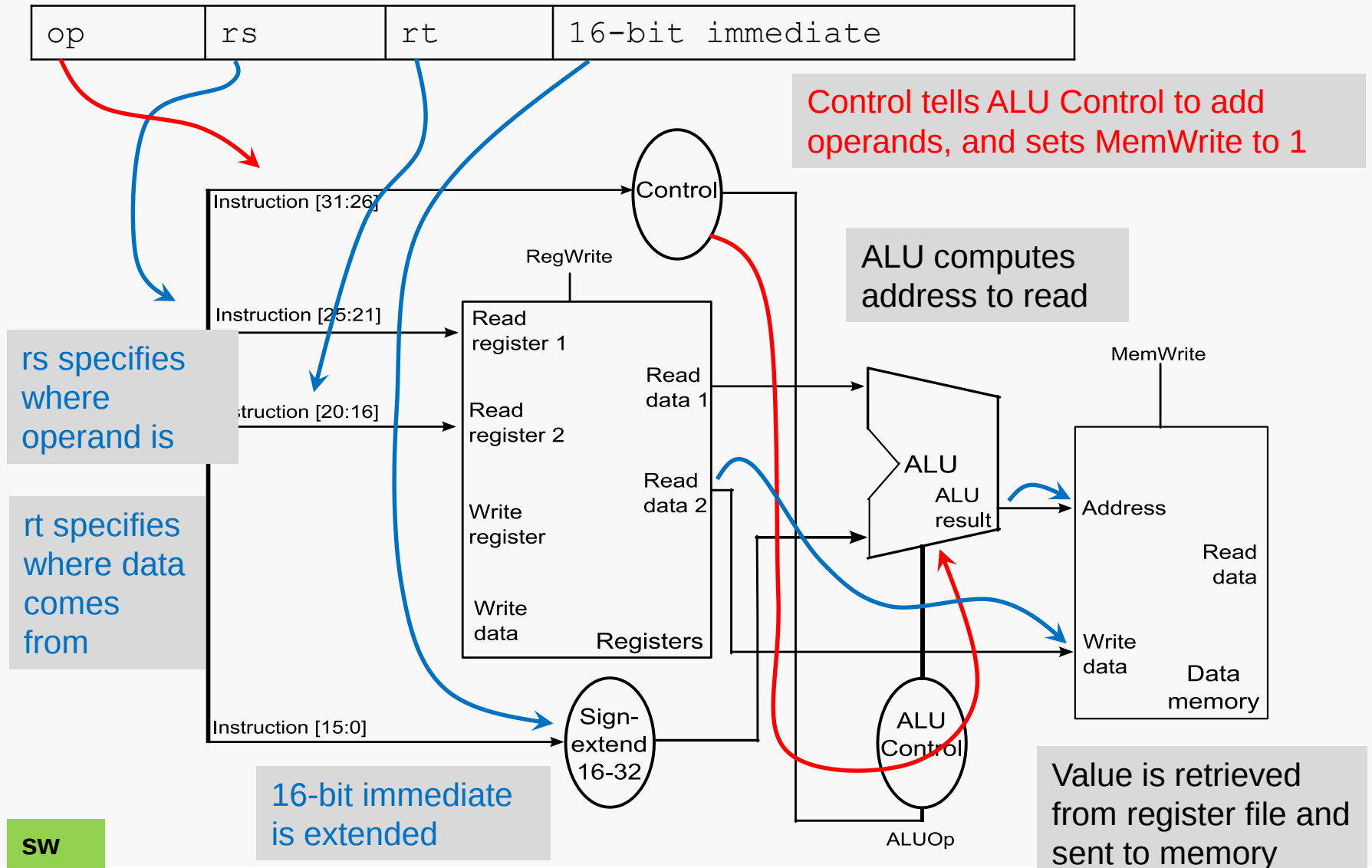
$$\text{Mem}[\text{GPR}[\text{rs}] + \text{imm}] = \text{GPR}[\text{rt}]$$



SW

In order to produce a complete datapath design, we must identify and deal with any conflicts.

First, consider the specification of the register numbers supplied to the register file.

They come from the current instruction, but using which bits?

	Read reg 1	Read reg 2	Write reg
R-type	25:21	20:16	15:11
load	25:21	not used	20:16
store	25:21	20:16	not used

OK

OK

Conflict

We have a conflict regarding the write register.

To resolve the conflict, we must be able to select one set of bits for R-type instructions and a different set of bits for the load instructions... how do we make a selection in hardware?

We also have a conflicts regarding the source of the write data and the source of the right (lower) operand to the ALU:

	Write data source	Right operand source
R-type	ALU output	register file
load	Data memory	sign-extend
store	not used	sign-extend


Conflict

Conflict

To resolve these conflicts, we must be able to:

- send the ALU output to the register file for R-type instructions, but send the data read from the memory unit to the register file for load instructions
- send the data read from the register file to the ALU for R-type instructions, but send the output from the sign-extender to the ALU for load and store instructions

 By adding three multiplexors, we can resolve the conflicts that we have identified and produce a design that will (almost) handle the R-type, load and store instructions we are considering.



add, sub, and, or, slt, lw, sw

We've identified quite a few necessary control signals in our design.

Which ones are two-valued? Do any require more than two values?

How should they be set?

The datapath cannot operate correctly unless every control signal is managed properly.

Two things to remember:

- Every line always carries a value. We may not know (or care) what it is in some cases. But there is always a value there.
- It doesn't matter what value a line carries if that value is never stored or used to make a decision. (Hence, we will find that we have *don't-care conditions*.)


R-type and load instructions require writing a value into a register, but the store instruction does not.

Writing a value modifies the state of the system, so it is *not a don't-care*.

So, we must manage the RegWrite signal accordingly:

	RegWrite
R-type	1
load	1
store	0

 Value at Write data is written to the Write register iff RegWrite is 1.




MemRead

- must be 1 for load instructions, since they copy a value from memory to a register
- might be a don't-care for R-type and store instructions... why? If not, should be 0.

MemWrite

 - must be 1 for store instructions, since they copy a value from a register to memory
- must be 0 for R-type and load instructions; otherwise they could modify a memory value that should not




	MemRead	MemWrite
R-type	?	0
load	1	0
store	?	1

RegDst

- must be 0 for load instructions
- must be 1 for R-type instructions
- don't-care for store instructions (why?)


see slide 10

 

ALUSrc

- must be 0 for R-type instructions
- must be 1 for load and store instructions


see slide 11

 

MemtoReg

- must be 1 for load instructions
- must be 0 for R-type instructions
- don't-care for store instructions (why?)

see slide 15

 

There are a lot of control signals, even in our simple datapath.

At this point, almost all of them are single-bit signals (i.e., they make a choice between two alternate actions).

The ALU control needs to be different because there are more than two choices for what it will actually do:

	ALU
R-type add sub and or slt	add subtract and or slt
load	add
store	add

So, the ALU will require a multi-bit control signal... why? How many bits?


This suggests separating the control logic into two modules:

- a master control module that determines the type of instruction being executed and sets the non-ALU control signals
- a secondary control module that manages the interface of the ALU itself

The master module will send :

- a specific selector pattern for the ALU if the instruction is not R-type; e.g., it sends the ADD selector pattern for `lw` and `sw` instructions
- a flag telling the secondary module to analyze the `funct` bits if the instruction is R-type

 We'll fill in the details of the two modules later, but for now we do know what each must do, at a high level.




add, sub, and, or, slt, lw, sw

```
if GPR[rs] == GPR[rt] then  
    PC = PC + 4 + (imm << 2)
```

Read two operands from the register file

Use the ALU to compare the operands: subtract and check Zero signal

...

 



...

Calculate the branch target address:

- Sign-extend displacement (immediate from instruction)
- Shift left 2 places (MIPS uses word displacement – why?)
- Add to PC + 4 (already calculated PC + 4 during the instruction fetch)

Send computed branch target address to the PC (if taken)
  
```
if GPR[rs] == GPR[rt] then  
    PC = PC + 4 + (imm << 2)
```



Examine the display below of a short MIPS assembly program, and the addresses at which the instructions will be loaded into memory when the program is executed:

If taken, a conditional branch causes the PC to be set to the address of the instruction that's the target of the branch:



address	assembly source code

	.text
0x00400000	main: addi \$s0, \$zero, 10
0x00400004	addi \$s1, \$zero, 20
0x00400008	j check
0x0040000C	repeat: sub \$s3, \$s1, \$s0
0x00400010	sra \$s3, \$s3, 1
0x00400014	beq \$s3, \$zero, exit
0x00400018	add \$s0, \$s0, \$s3
0x0040001C	check: bne \$s0, \$s1, repeat
0x00400020	exit: li \$v0, 10
0x00400024	syscall

address	assembly source code

	.text
0x00400000	main: addi \$s0, \$zero, 10
0x00400004	addi \$s1, \$zero, 20
0x00400008	j \$check
0x0040000C	repeat: sub \$s3, \$s1, \$s0
0x00400010	sra \$s3, \$s3, 1
0x00400014	beq \$s3, \$zero, exit
0x00400018	add \$s0, \$s0, \$s3
0x0040001C	check: bne \$s0, \$s1, repeat
0x00400020	exit: li \$v0, 10
0x00400024	syscall

First of all, note that all the addresses are multiples of 4*.

Therefore, the "distance" between two instructions is always a multiple of 4.

***QTP: why isn't this surprising?**

The immediate we store for a `beq` instruction is determined by the "distance" from the `beq` instruction to the instruction that is the target of the branch.

address	assembly source code			

. . .				
0x0040000C	repeat:	sub	\$s3, \$s1, \$s0	
. . .				
0x0040001C	check:	bne	\$s0, \$s1, repeat	
0x00400020	exit:	li	\$v0, 10	
. . .				



However, while `bne` is being fetched:

- we have already computed `PC + 4`
- which is the address of the next instruction in memory
- so we need to compute the distance relative to the next instruction

And note that this computation is done by the assembler when it creates the machine code representation of the instruction, not at runtime.

address	assembly source code

. . .	
0x0040000C	repeat: sub \$s3, \$s1, \$s0
. . .	
0x0040001C	check: bne \$s0, \$s1, repeat
0x00400020	exit: li \$v0, 10
. . .	

Here, that "distance" is $0x0C - 0x20 = -0x14$.

In 16-bit 2's complement, 0x14 represented as: 00000000 00010100

If the "distance" always ends in 00, there's no reason to store that 00 in the instruction...

Do we gain anything if we don't store those two 0's in the instruction?

address	assembly source code

. . .	
0x0040000C	repeat: sub \$s3, \$s1, \$s0
. . .	
0x0040001C	check: bne \$s0, \$s1, repeat
0x00400020	exit: li \$v0, 10
. . .	

Yes. We can store a 16-bit "distance" in the instruction, but effectively use an 18-bit "distance" at runtime.

That means that a conditional branch can "branch" farther... which is a gain.

16-bit 2's complement range: -2^{15} to $2^{15}-1$

18-bit 2's complement range: -2^{17} to $2^{17}-1$

Now, consider the machine code for our example:

address	machine code
-----	-----
. . .	
0x0040000C	} -0x14
. . .	
0x0040001C	
0x00400020	000101 10000 10001 111111111111011
. . .	


target → 0x0040000C

bne → 0x00400020

The immediate in the `beq` instruction is: 1111111111111011

That's -5. If we shift that left by 2 bits (multiply by 4), we get -20 (0x14).

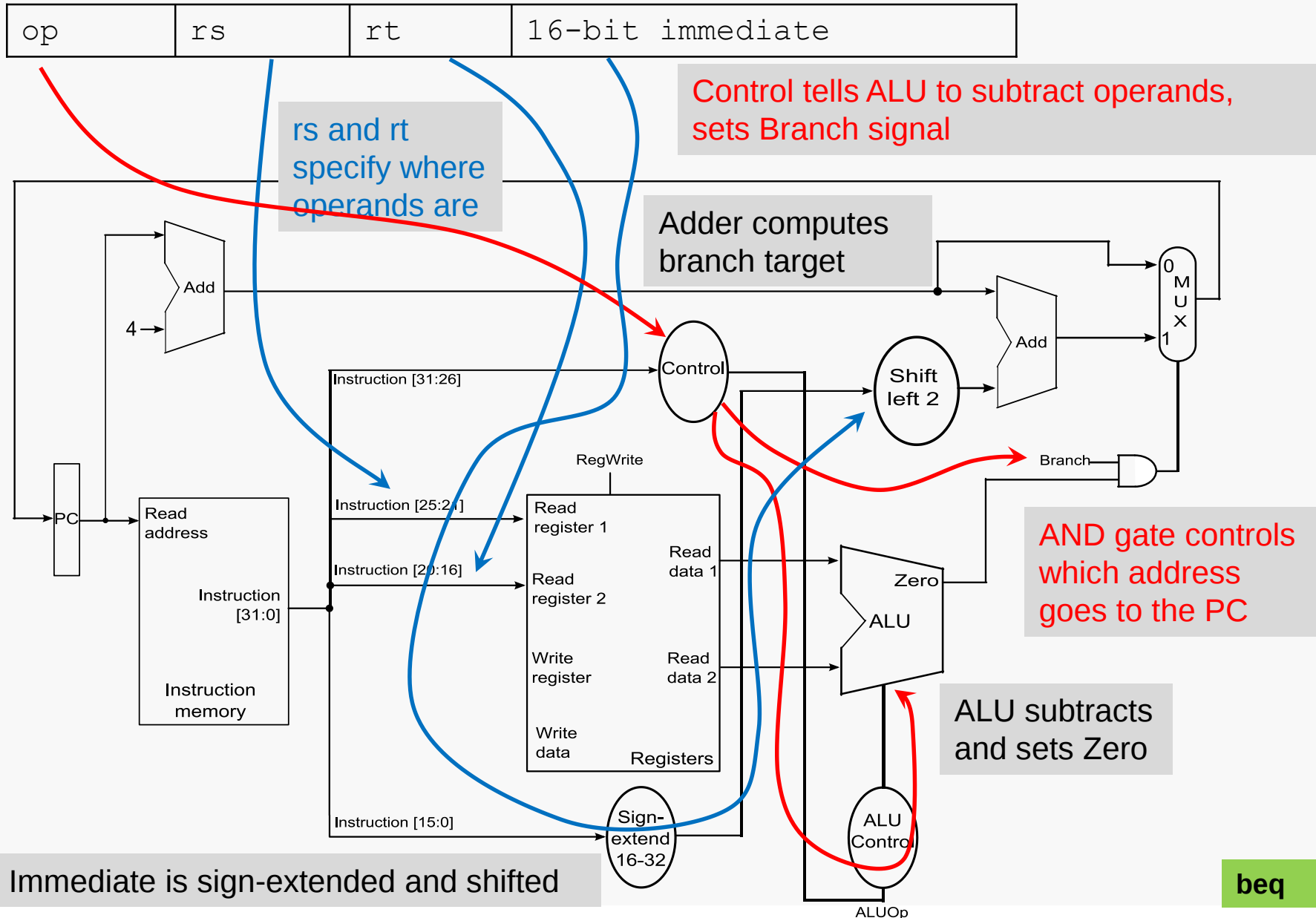If we add -0x14 to the address 0x00400020, we get 0x0040000C, which is the target address we need.




beq

Calculate the jump target address:

$$PC = (PC+4)[31:28] \mid (IR[25:0] \ll 2)$$

- Shift left 2 places (just as with branch target address calculation)
- Concatenate with PC + 4[31:28] (already calculated PC + 4 during the instruction fetch)

 Send computed jump target address to the PC




The calculation of the jump target address is similar to the calculation of the branch target address (`beq`).

The MIPS model is to view memory as a sequence of 256 MB segments.

The starting address of the current memory segment is given by the high 4 bits of $PC + 4$.*


Now, 256 MB can be addressed by 28-bit addresses.*

 
For jump (`j`) instructions, the 26-bit immediate is shifted 2 bits to the left, yielding a 28-bit offset, which is then added to the starting address of the current memory segment.



*QTP: why?

4GB address range

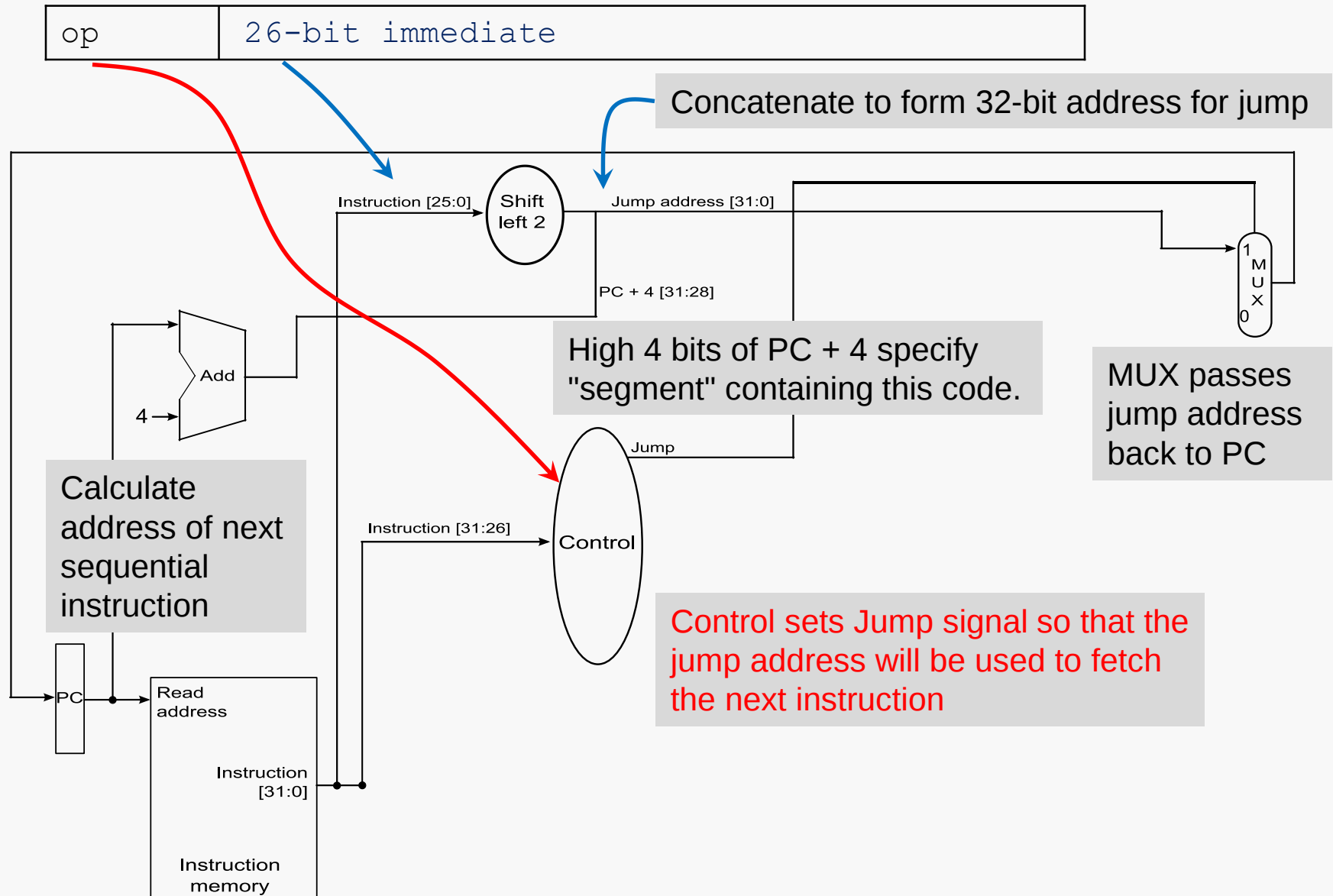

 

The unified datapath that we have designed:

- illustrates many of the logical issues that must be solved in designing any datapath
- can be extended to support additional instructions (easily for some, less so for others)
- is fundamentally unsatisfactory in that it requires a single clock cycle be long enough for every path within the datapath to stabilize before the next instruction is fetched

We may explore the second issue in exercises.

The third issue can only be dealt with by transforming the design to incorporate a pipeline.